
 


# Design

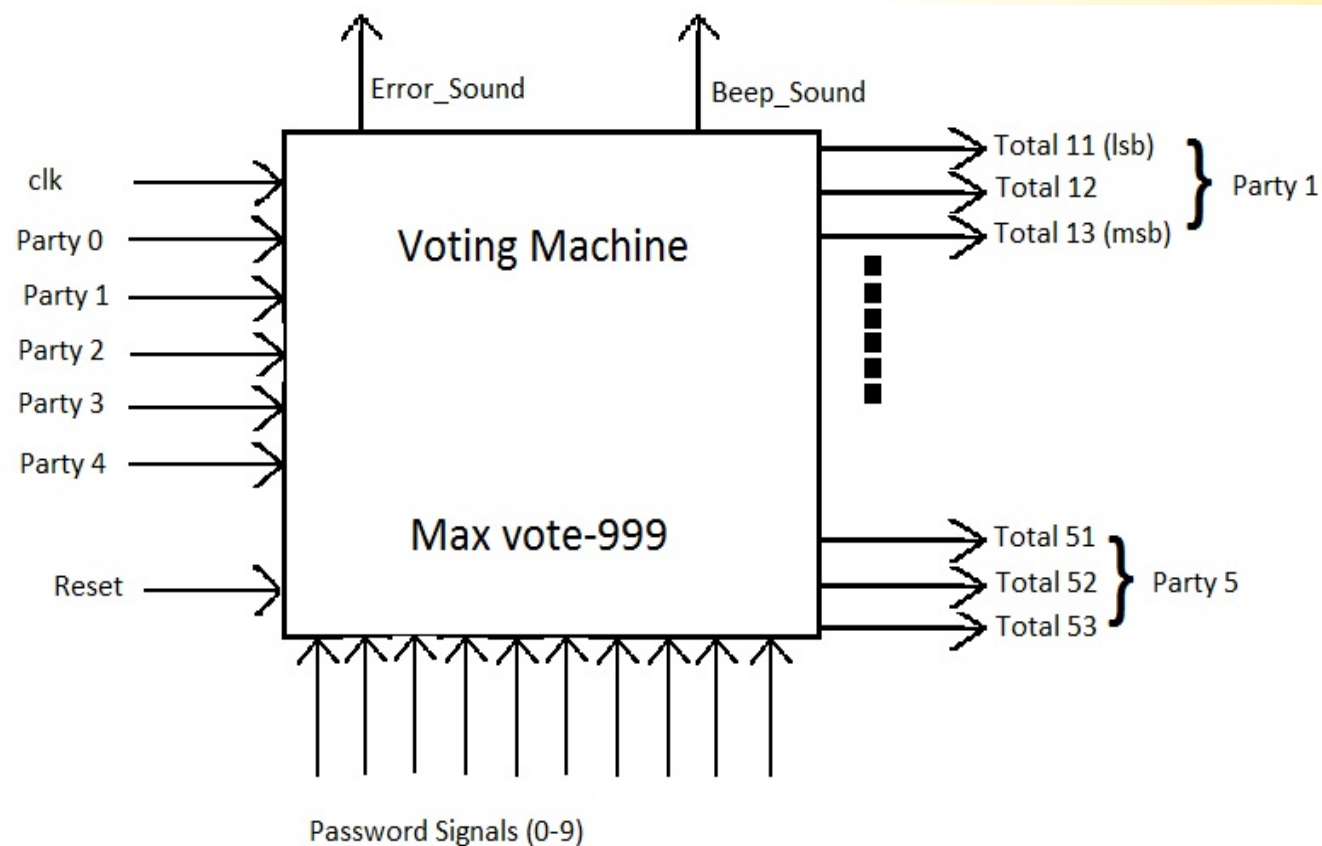

# Black- Box of Machine



# Input Signals to Machine

1. Enable
2. Party(0-4)
3. Reset
4. Password

# 1.Enable

The function of enable input is to on and off the machine. It will be controlled manually by the officials. They can on and off the Machine as per their requirement .

When Machine will be turned off the vote count will be stored in its memory and can be accessed later on.

When the input to enable is “0” then the machine is on i.e it will count the votes and when the input is “1” then it is off and will not count any vote.

## 2. Party(0-4)

These are the input buttons on the machine to vote for a particular party.

When button is pressed the vote will be counted.

It doesn't matter how longer you press the button it will count the single vote for one time press as it will count on the falling edge.

Party 0- First Party

Party 1- Second Party

Party 2- Third Party

Party 3- Fourth Party

Party 4- Fifth Party

## 3.Reset

This input will not be accessed from the outer body of the machine as it will reset the whole machine i.e it will be used to renew the machine for further elections so it will be accessed by inside the machine.

Vote count will become zero when the input to reset will “1”.

## 4.Password

(Pass 0-9)

This is password input of the voting machine. Pass key (0-9) will take input of the password by which the officials will gain access to vote count.

When password is will be entered and display button will be pressed the the machine will show vote count on the 7-segment display.

# Output Signals

1.Error sound
2.Beep sound
3.7-segment display(total)

# 1.Error Sound

It will produce error sound when there will be any in-discrepancy in the machine such as when someone will press 2 party buttons simultaneously.

When Error-sound is produced then that vote will not be counted.



## 2. Beep sound

This output will produce a beep sound i.e when their will be normal input to machine and everything else is good. The vote with beep sound will be counted.

## 3. 7-Segment display(total)

This is the output to the 7 segment LED display which will be accessed by entering password .It will display the total vote count of all the parties.

total11	}	->LSB
total12		
total13		
		->MSB

# VHDL-code

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity voting_machine is  
  port( Clock_enable_B: in std_logic;  
        party :in std_logic_vector(0 to  
4);
```

```
        beep_sound :out std_logic ;  
        error_sound: out std_logic;  
        Reset: in std_logic;  
        pass0:in std_logic;  
        pass1:in std_logic;  
        pass2:in std_logic;  
        pass3:in std_logic;  
        pass4:in std_logic;  
        pass5:in std_logic;  
        pass6:in std_logic;
```

```
        pass7:in std_logic;  
        pass8:in std_logic;  
        pass9:in std_logic;
```

```
        total11 :out std_logic_vector(0 to 6);  
        total12:out std_logic_vector(0 to 6);  
        total21 :out std_logic_vector(0 to 6);  
        total22:out std_logic_vector(0 to 6);  
        total31 :out std_logic_vector(0 to 6);  
        total32:out std_logic_vector(0 to 6);  
        total41 :out std_logic_vector(0 to 6);  
        total42:out std_logic_vector(0 to 6);  
        total51 :out std_logic_vector(0 to 6);  
        total52:out std_logic_vector(0 to 6);  
        total13:out std_logic_vector(0 to 6);  
        total23 :out std_logic_vector(0 to 6);  
        total33:out std_logic_vector(0 to 6);
```

```
total43 :out std_logic_vector(0 to 6);  
    total53:out std_logic_vector(0 to 6));
```

```
end voting_machine;
```

```
architecture voting_archi of voting_machine is  
component BCD_party is
```

```
port( Clock_enable_B: in std_logic;  
      party: in std_logic;  
      Reset: in std_logic;  
      display: in std_logic;  
      total1 :out std_logic_vector(0 to 6);  
      total3 :out std_logic_vector(0 to 6);  
      carry: out std_logic;  
      total2:out std_logic_vector(0 to 6));
```

```
end component;
```

```
signal carry1,carry2,carry3,carry4,carry5,display: std_logic;
```

```
signal tparty: std_logic_vector(0 to 4);
```

```
begin
```

```
Stage1: BCD_party port map(clock_enable_B,tparty(0),Reset,display,total11,total13,carry1,total12);
```

```
Stage2: BCD_party port
```

```
map(clock_enable_B,tparty(1),Reset,display,total21,total23,carry2,total22);
```

Stage3: BCD\_party port

```
map(clock_enable_B,tparty(2),Reset,display,total31,total33,carry3,total32);
```

Stage4: BCD\_party port

```
map(clock_enable_B,tparty(3),Reset,display,total41,total43,carry4,total42);
```

Stage5: BCD\_party port

```
map(clock_enable_B,tparty(4),Reset,display,total51,total53,carry5,total52);
```

```
display <=((not pass0)and (not pass1) and( pass2)and ( pass3)and(not pass4)and (
pass5)and( pass6)and( pass7)and(not pass8)and( pass9));
```

```
process(party)
```

```
begin
```

```
case party is
```

```
when "10000" => beep_sound <='1';
```

```
when "01000" => beep_sound <='1';
```

```
when "00100" => beep_sound <='1';
```

```
when "00010" => beep_sound <='1';
```


```
when "00001" => beep_sound <='1';
```

```
when others => beep_sound<='0';
end case;
end process;
process(party)
begin
case party is
when "10000" => error_sound <='0';
when "01000" => error_sound <='0';
when "00100" => error_sound <='0';
when "00010" => error_sound <='0';
when "00001" => error_sound <='0';
when "00000" => error_sound <='0';
--- if some one press more button the error sound
will given
when others => error_sound<='1';
end case;
end process;
process(party)
begin
case party is
when "10000" => tparty <="10000";
when "01000" => tparty <="01000";
```

```
when "00100" => tparty <="00100";
when "00010" => tparty <="00010";
when "00001" => tparty <="00001";
--- if error came or no button pushed then no vote will
calculated
when others => tparty<="00000";
end case;
end process;

end voting_archi;
```

# Waveform of Machine

 



44
52
60
68
76
84
92
100
108
116
124
132

+	total21
+	total22
+	total23
+	total31
+	total32
+	total33
+	total41
+	total42
+	total43
+	total51
+	total52
+	total53

B 1'	1111111	1001111
B 1'	1111111	0000001
B 1'	1111111	0000001
B 1'	1111111	0000110
B 1'	1111111	0000001
B 1'	1111111	0000001
B 1'	1111111	0010010
B 1'	1111111	0000001
B 1'	1111111	0000001
B 1'	1111111	0010010
B 1'	1111111	0000001
B 1'	1111111	0000001

1
0
0
3
0
0
2
0
0
2
0
0


001

003

002


002

# RTL View

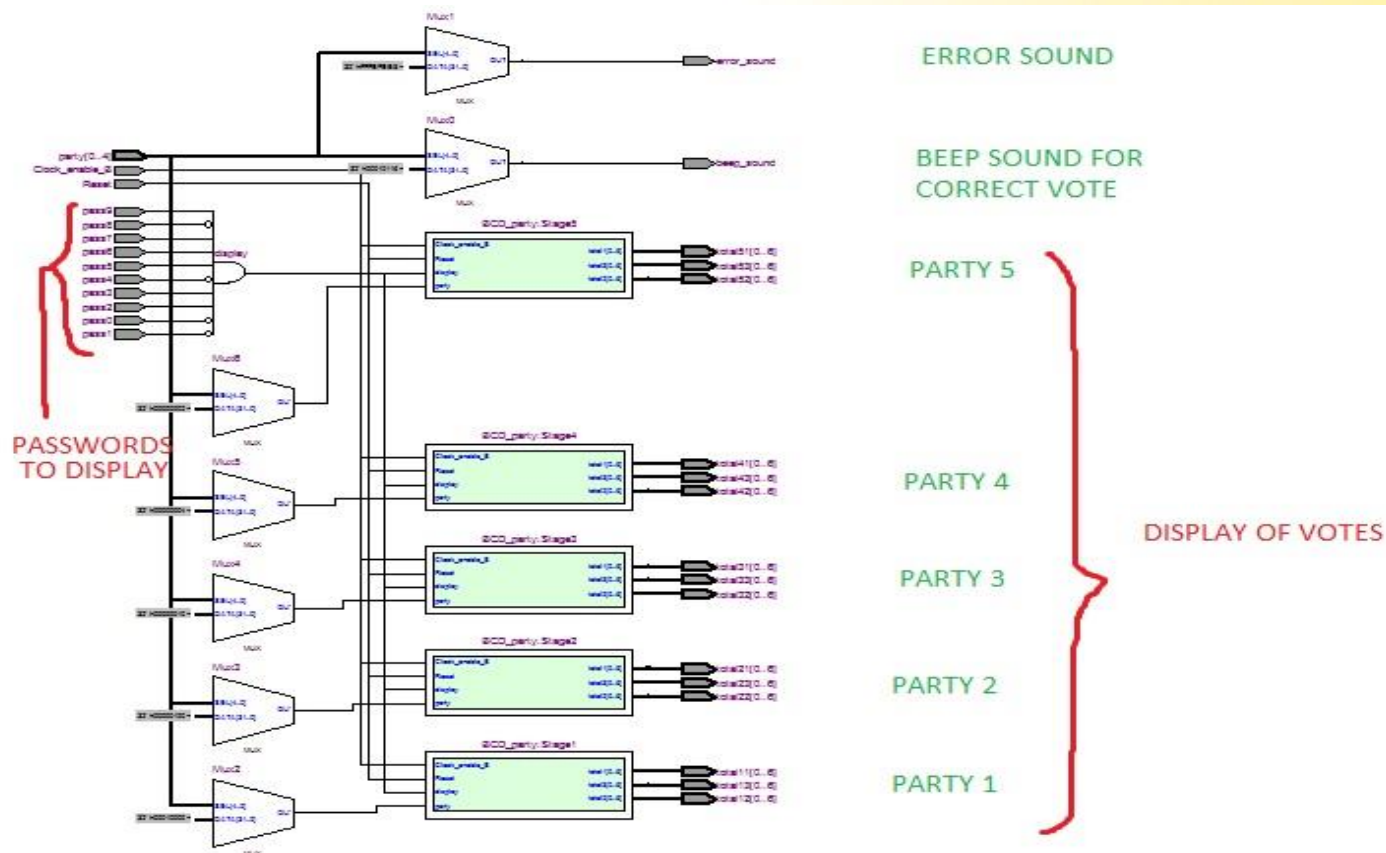



# BCD-PARTY

 

# INPUT

## **Clock enable:**

**When the input is low it will start counting otherwise it will stop working but our previous data will be conserved**

## **Party Button:**

**Actually a permanent clock signal(low) is generated and when the first voter will press the button the clock will be high and when the voter will leave the button the clock will be low again and again when the second voter will press the button the clock will be high again and the voter will leave the button clock will be low again and this process will continue and each falling edge of the clock will be counted as 1 vote by the counter**

## **Reset:**

**When input will be high all data will reset**

## **Display:**

**When input will be high it will display the total with the help of three 7-segment display.**

## **Output**

**total1(msb), total2, total3(lsb) will display the total votes of a particular party**

# VHDL CODE FOR BCD PARTY

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity BCD_party is
```

```
port( Clock_enable_B: in std_logic;
```

```
      party: in std_logic;
```

```
      Reset: in std_logic;
```

```
      display: in std_logic;
```

**total1 :out std\_logic\_vector(0 to 6);**

**total3 :out std\_logic\_vector(0 to 6);**

**carry: out std\_logic;**

**total2:out std\_logic\_vector(0 to 6));**

**end BCD\_party;**

**architecture party\_archi of BCD\_party is**

**component BCD\_display is**

**port( Clock\_enable\_B: in std\_logic;**

**party: in std\_logic;**

**Reset: in std\_logic;**

**display: in std\_logic;**

**carry:out std\_logic;**

**total :out std\_logic\_vector(0 to 6));**

**end component;**

**signal party\_next:std\_logic;**

**signal party\_next1:std\_logic;**

**begin**

**stage1 : BCD\_display port map(Clock\_enable\_B ,party ,Reset,display,party\_next,total1);**

**stage2 : BCD\_display port map(Clock\_enable\_B ,party\_next ,Reset,display,party\_next1,total2);**


**stage3 : BCD\_display port map(Clock\_enable\_B ,party\_next1 ,Reset,display,carry,total3);**

**end party\_archi;**

# BCD PARTY WAVE FORM


Simulation Waveforms

Simulation mode: Timing

 


The party (clock signal) is high 11 times that means 11 voters has voted to that party  
So total1(lsb) will be 1001111 that indicates 1 on 7 segment display i.e 1 and similarly  
total2 will display 1 and toatl 3 will display 0 on three 7-segment display

# BCD PARTY RTL VIEW

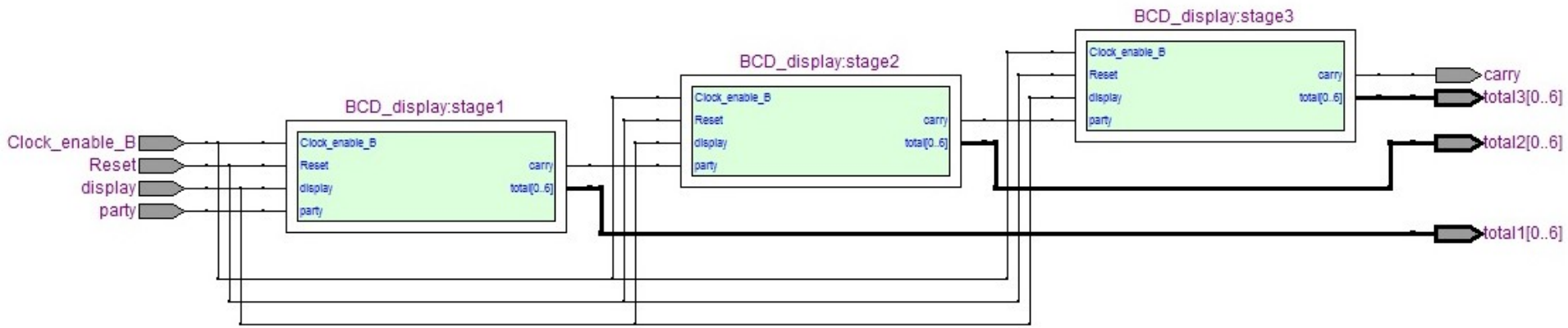



# BCD-DISPLAY

 

The output total1 will show LSB of the resultant vote and if the LSB is 10 then LSB will become 0 and 1 will be added to the total2 i.e is the second bit. Since maximum voters are 999 so we will use three seven segment display to show the final votes of a particular party

## VHDL CODE FOR BCD-DISPLAY

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BCD_display is
  port( Clock_enable_B: in std_logic;
        party: in std_logic;
        Reset: in std_logic;
        display: in std_logic;
        carry: out std_logic;
        total :out std_logic_vector(0 to 6));
```

**end BCD\_display;**

**architecture BCDARCHI of BCD\_display is**

**signal temp: std\_logic\_vector(0 to 3);**

**signal segment7 :std\_logic\_vector(0 to 6);**

**begin**

**process(party,Reset)**

**begin**

**if Reset='1' then**

**temp <= "0000";elseif(falling\_edge(party)) then**

**if Clock\_enable\_B='0' then**

**if temp="1001" then**

**temp<="0000";**

**Else**

**temp <= temp + 1;**

**end if;**

**end if;**

**end if;**

**end process;**

**process (party,temp,display)**

**BEGIN**

**case temp is**

**when "0000"=> segment7 <="0000001"; -- '0'**

**when "0001"=> segment7 <="1001111"; -- '1'**

**when "0010"=> segment7 <="0010010"; -- '2'**

**when "0011"=> segment7 <="0000110"; -- '3'**

**when "0100"=> segment7 <="1001100"; -- '4'**

**when "0101"=> segment7 <="0100100"; -- '5'**

**when "0110"=> segment7 <="0100000"; -- '6'**

**when "0111"=> segment7 <="0001111"; -- '7'**

**when "1000"=> segment7 <="0000000"; -- '8'**

**when "1001"=> segment7 <="0000100"; -- '9'**

**--nothing is displayed when a number more than 9 is given as input.**

**when others=> segment7 <="1111111";**

**end case;**

**if display='1' then**

**total <=segment7 ;**

**else total <= "1111111";**


**end if;**

**end process;**


**carry <=(( temp(0))and (not temp(1))and( temp(2))and(not temp(3)));**

**end BCDARCHI;**

# BCD DISPLAY WAVEFORM

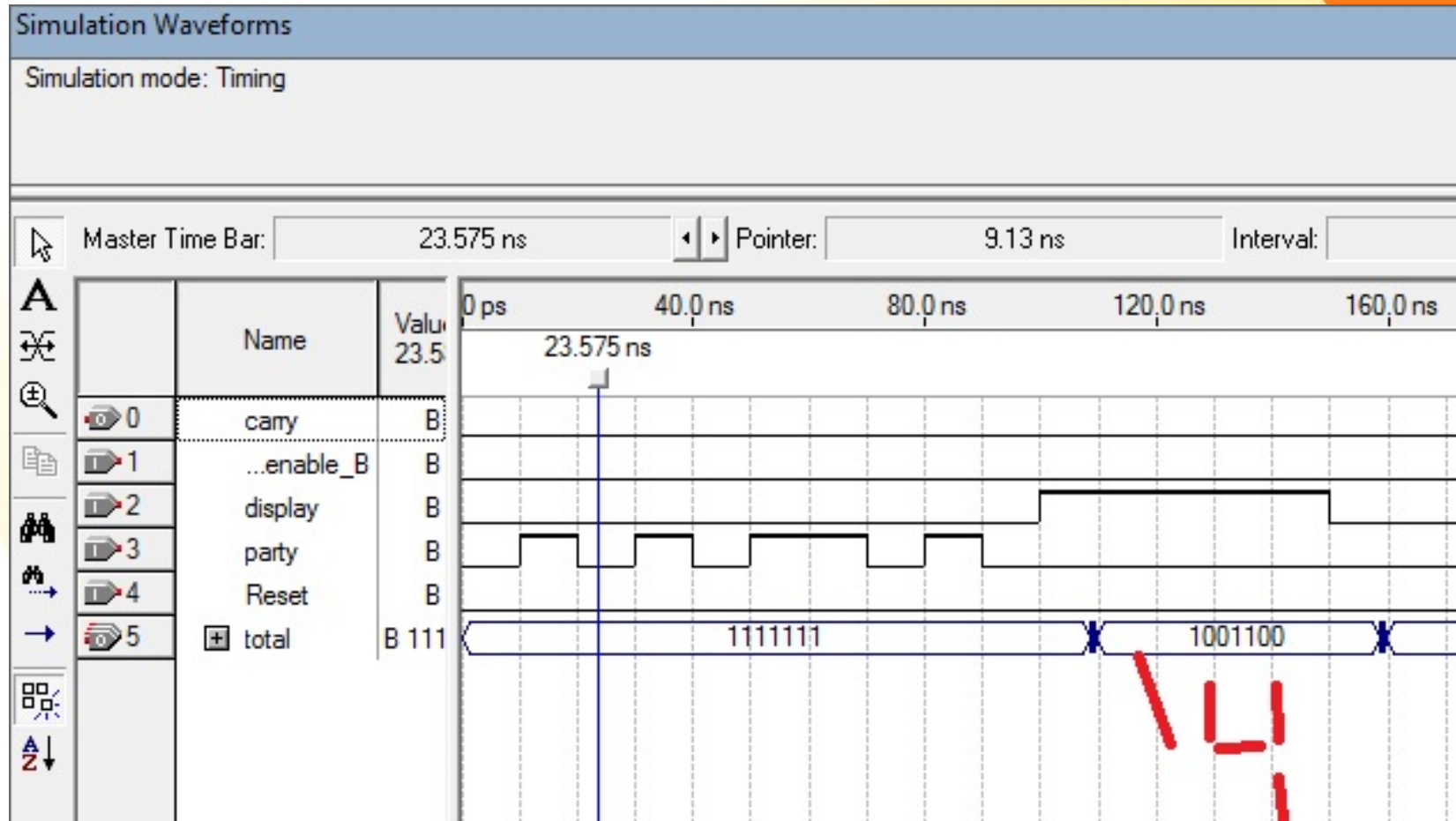


## RTL VIEW of DISPLAY

 



## 7-segment display

 

**7-segment display for decimal no's 0 to 9**

**Input 1 = OFF & Input 0 = ON**

## TRUTH TABLE FOR 7-SEGMENT DISPLAY

Segments Inputs							7 Segment Display Output
a	b	c	d	e	f	g	
0	0	0	0	0	0	1	0
1	0	0	1	1	1	1	1
0	0	1	0	0	1	0	2
0	0	0	0	1	1	0	3
1	0	0	1	1	0	0	4
0	1	0	0	1	0	0	5
0	1	0	0	0	0	0	6
0	0	0	1	1	1	1	7
0	0	0	0	0	0	0	8
0	0	0	0	1	0	0	9



END